

# SoC Design Laboratory Lab3

EE 112061545 Chih-ling Wu

[SoC Lab3 Github Link](#)

## 1. Introduction:

In this lab, we implemented a FIR system in Verilog, using AXI-Lite interfaces for coefficients and Stream interfaces for data. We also collaborated with a BRAM module to handle data efficiently. The core focus of this lab is to master the control of handshake signals within these protocols and to create a well-designed data flow.

## 2. System Block diagrams:

 


Fig1. FIR module block diagram

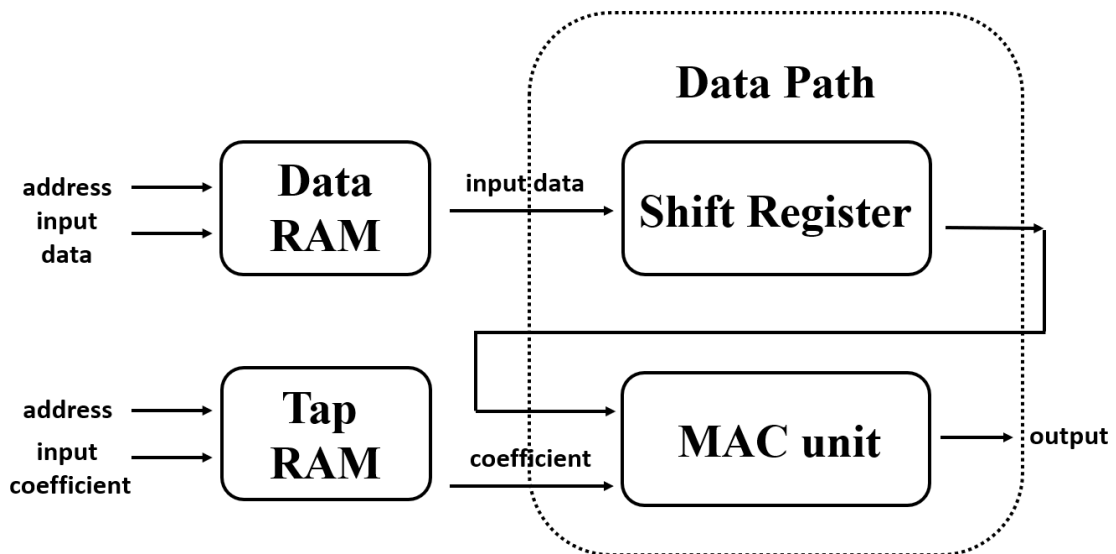


Fig2. Data path block diagram breakdown

(1) Dataflows:

- Shift Register:

Input data is stored and shifted as new data arrives.

- MAC:

Performing the multiplication and addition operations for the FIR filter.

- Data RAM:

Storing input data.

- Tap RAM:

Storing filter coefficients (tap parameters).

(2) Control signals:

- Handshake Signals:

Facilitating communication with the AXI-Lite interface and the stream interface.

- Flags:

Indicating the configuration and operation status of the filter (ap\_start, ap\_idle, ap\_done).

- State Machine:

To control the operation of the FIR filter with states (IDLE, LOAD, MAC, DONE).

## FSM for fir computing

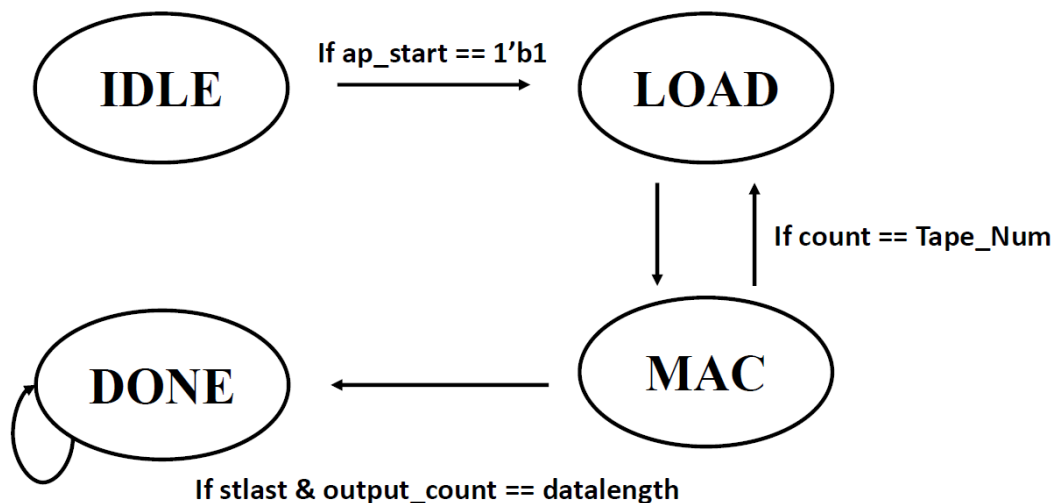


Fig3. Design for finite state machine for fir computing

### 3. Operations:

#### (1) How to Receive Data-In and Tap Parameters and Place into SRAM?

Input data is received through the "Stream Interface" (ss\_tvalid, ss\_tdata, ss\_tlast). Data is loaded into the "Data RAM" for processing and stored in the "Shift Register."

Filter coefficients (tap parameters) are configured through the AXI-Lite interface using write transactions. The coefficients are loaded into the "Tap RAM" for use in the FIR filter.

#### (2) How to Access Shift Register and Tap RAM to Do Computation?

During the "MAC" state, the FIR filter retrieves data from the "Shift Register" to perform the computation. The data is used as input to the "MAC Unit."

The FIR filter accesses the "Tap RAM" to retrieve the filter coefficients (tap parameters) corresponding to the current computation. These coefficients are also used by the "MAC Unit" for the multiplication operation.

#### (3) How to generate ap signals?

ap\_start: This signal is generated when the coefficient read is done. It is set to 1 for one clock cycle when the address for reading coefficients is detected.

ap\_done: This signal is generated based on conditions, including the output count matching the data length and the current state not being IDLE.

ap\_idle: It is set to 1 when the FIR filter is idle or not actively processing data. It transitions to 0 when a new operation starts (ap\_start is 1) and returns to 1 when the operation is complete.

#### (4) How to generate handshake signals in two interfaces?

##### ※ AXI-Lite Interface Handshake Signals:

- awready and arready (write and Read Ready): These signals indicate readiness to accept addresses for write and read operations, respectively. They are updated based on the presence of valid address signals.

- wready and rready (write and Read Ready): These signals reflect readiness to accept data for writing or to send data for reading. They are directly derived from the presence of valid data signals.

##### ※Stream Interface Handshake Signals:

- ss\_tready (ready to Receive Data): This signal represents readiness to receive data through the Stream interface. Its status depends on the current state and the

presence of valid data.

- **sm\_tvalid** (valid for Sending Back Output Data): This signal indicates when the module is ready to send back output data through the Stream interface. It becomes valid when specific conditions are met, allowing the module to transmit data.

#### 4. Simulation waveform & results:

(1) Coefficient program, and read back:

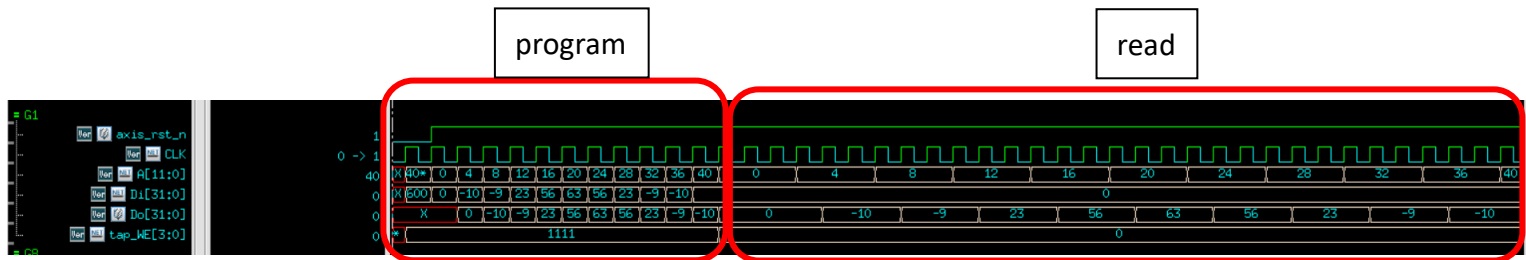


Fig4. Coefficient read / program waveform

```

-----Start simulation-----
---Start the data input(AXI-Stream)---
---Start the coefficient input(AXI-lite)---
Check Coefficient ...
OK: exp =      0, rdata =      0
OK: exp =    -10, rdata =    -10
OK: exp =     -9, rdata =     -9
OK: exp =     23, rdata =     23
OK: exp =     56, rdata =     56
OK: exp =     63, rdata =     63
OK: exp =     56, rdata =     56
OK: exp =     23, rdata =     23
OK: exp =     -9, rdata =     -9
OK: exp =    -10, rdata =    -10
OK: exp =      0, rdata =      0

```

Fig5. Coefficient read / program simulation result

(2) Data-in stream-in:

 


Fig6. Data stream in waveform

(3) Data-out stream-out:

 


Fig7. Data stream out waveform

```

[PASS] [Pattern 568] Golden answer: -6588, Your answer: -6588
[PASS] [Pattern 569] Golden answer: -6405, Your answer: -6405
[PASS] [Pattern 570] Golden answer: -6222, Your answer: -6222
[PASS] [Pattern 571] Golden answer: -6039, Your answer: -6039
[PASS] [Pattern 572] Golden answer: -5856, Your answer: -5856
[PASS] [Pattern 573] Golden answer: -5673, Your answer: -5673
[PASS] [Pattern 574] Golden answer: -5490, Your answer: -5490
[PASS] [Pattern 575] Golden answer: -5307, Your answer: -5307
[PASS] [Pattern 576] Golden answer: -5124, Your answer: -5124
[PASS] [Pattern 577] Golden answer: -4941, Your answer: -4941
[PASS] [Pattern 578] Golden answer: -4758, Your answer: -4758
[PASS] [Pattern 579] Golden answer: -4575, Your answer: -4575
[PASS] [Pattern 580] Golden answer: -4392, Your answer: -4392
[PASS] [Pattern 581] Golden answer: -4209, Your answer: -4209
[PASS] [Pattern 582] Golden answer: -4026, Your answer: -4026
[PASS] [Pattern 583] Golden answer: -3843, Your answer: -3843
[PASS] [Pattern 584] Golden answer: -3660, Your answer: -3660
[PASS] [Pattern 585] Golden answer: -3477, Your answer: -3477
[PASS] [Pattern 586] Golden answer: -3294, Your answer: -3294
[PASS] [Pattern 587] Golden answer: -3111, Your answer: -3111
[PASS] [Pattern 588] Golden answer: -2928, Your answer: -2928
[PASS] [Pattern 589] Golden answer: -2745, Your answer: -2745
[PASS] [Pattern 590] Golden answer: -2562, Your answer: -2562
[PASS] [Pattern 591] Golden answer: -2379, Your answer: -2379
[PASS] [Pattern 592] Golden answer: -2196, Your answer: -2196
[PASS] [Pattern 593] Golden answer: -2013, Your answer: -2013
[PASS] [Pattern 594] Golden answer: -1830, Your answer: -1830
[PASS] [Pattern 595] Golden answer: -1647, Your answer: -1647
OK: exp = 0, rdata = 0
[PASS] [Pattern 596] Golden answer: -1464, Your answer: -1464
-----End the data input (AXI-Stream)-----
[PASS] [Pattern 597] Golden answer: -1281, Your answer: -1281
[PASS] [Pattern 598] Golden answer: -1098, Your answer: -1098
[PASS] [Pattern 599] Golden answer: -915, Your answer: -915
OK: exp = 2, rdata = 6
OK: exp = 4, rdata = 6
-----
-----Congratulations! Pass-----
Simulation complete via $finish(1) at time 78675 NS + 0
./tb/fir_tb.v:200 $finish;
ncsim> exit
[chihlinggg@node01 fir]$

```

Fig8. Data-out match golden results

(4) RAM access control:

 


Fig9. Tap RAM access control

 


Fig10. Data RAM access control

Fig11. FSM transition

## 5. Resource Usage:

```

Start RTL Component Statistics
-----
Detailed RTL Component Info :
+---Adders :
    2 Input      32 Bit      Adders := 2
    2 Input      12 Bit      Adders := 2
    2 Input      10 Bit      Adders := 1
    2 Input       4 Bit      Adders := 1
+---Registers :
           32 Bit      Registers := 27
           10 Bit      Registers := 1
           4 Bit       Registers := 1
           2 Bit       Registers := 1
           1 Bit       Registers := 6
+---Multipliers :
           32x32      Multipliers := 1
+---Muxes :
    2 Input      32 Bit      Muxes := 9
    2 Input      12 Bit      Muxes := 3
    2 Input       6 Bit      Muxes := 1
    3 Input       4 Bit      Muxes := 1
    2 Input       4 Bit      Muxes := 2
    3 Input       2 Bit      Muxes := 1
    4 Input       2 Bit      Muxes := 2
    2 Input       1 Bit      Muxes := 6
    3 Input       1 Bit      Muxes := 1
    13 Input      1 Bit      Muxes := 11
-----
Finished RTL Component Statistics
-----

```

Fig12. Resource: one 32bit multiplier and one 32bit adder

## 1. Slice Logic

Site Type	Used	Fixed	Prohibited	Available	Util%
Slice LUTs*	516	0	0	53200	0.97
LUT as Logic	516	0	0	53200	0.97
LUT as Memory	0	0	0	17400	0.00
Slice Registers	887	0	0	106400	0.83
Register as Flip Flop	887	0	0	106400	0.83
Register as Latch	0	0	0	106400	0.00
F7 Muxes	0	0	0	26600	0.00
F8 Muxes	0	0	0	13300	0.00

Fig13. Resource: LUT and FFs

## 2. Memory


Site Type	Used	Fixed	Prohibited	Available	Util%
Block RAM Tile	0	0	0	140	0.00
RAMB36/FIFO*	0	0	0	140	0.00
RAMB18	0	0	0	280	0.00

Fig14. No use of BRAM in module

## 6. Timing Reports:

Max Delay Paths				Clock period: 12ns
Slack (MET) :	0.037ns (required time - arrival time)			
Source:	araddr[5] (input port clocked by axis_clk {rise@0.000ns fall@6.000ns period=12.000ns})			
Destination:	tap_A[11] (output port clocked by axis_clk {rise@0.000ns fall@6.000ns period=12.000ns})			
Path Group:	axis_clk			
Path Type:	Max at Slow Process Corner			
Requirement:	12.000ns (axis_clk rise@12.000ns - axis_clk rise@0.000ns)			
Data Path Delay:	7.128ns (logic 4.901ns (68.763%) route 2.226ns (31.237%))			
Logic Levels:	6 (CARRY4=2 IBUF=1 LUT1=1 LUT4=1 OBUF=1)			
Input Delay:	2.400ns			
Output Delay:	2.400ns			
Clock Uncertainty:	0.035ns ((TSJ^2 + TIJ^2)^1/2 + DJ) / 2 + PE			
Total System Jitter	(TSJ): 0.071ns			
Total Input Jitter	(TIJ): 0.000ns			
Discrete Jitter	(DJ): 0.000ns			
Phase Error	(PE): 0.000ns			
Location	Delay type	Incr(ns)	Path(ns)	Netlist Resource(s)
(clock axis_clk rise edge)				
	input delay	0.000	0.000 r	
		2.400	2.400	
	net (fo=0)	0.000	2.400 f	araddr[5] (IN)
		0.000	2.400	araddr[5]
	IBUF (Prop_ibuf_I_O)	0.972	3.372 f	araddr_IBUF[5]_inst/I
	net (fo=44, unplaced)	0.800	4.171	araddr_IBUF[5]_inst/O
				araddr_IBUF[5]
	LUT1 (Prop_lut1_I0_O)	0.124	4.295 r	tap_A_OBUF[7]_inst_i_9/I0
	net (fo=1, unplaced)	0.000	4.295	tap_A_OBUF[7]_inst_i_9/O
				tap_A_OBUF[7]_inst_i_9_n_0
				tap_A_OBUF[7]_inst_i_3/S[1]
	CARRY4 (Prop_carry4_S[1]_CO[3])	0.533	4.828 r	tap_A_OBUF[7]_inst_i_3/CO[3]
	net (fo=1, unplaced)	0.009	4.837	tap_A_OBUF[7]_inst_i_3_n_0
				tap_A_OBUF[11]_inst_i_4/CI
	CARRY4 (Prop_carry4_CI_O[3])	0.331	5.168 r	tap_A_OBUF[11]_inst_i_4/O[3]
	net (fo=1, unplaced)	0.618	5.786	addr_reg02_in[11]
				tap_A_OBUF[11]_inst_i_1/I3
	LUT4 (Prop_lut4_I3_O)	0.307	6.093 r	tap_A_OBUF[11]_inst_i_1/O
	net (fo=1, unplaced)	0.800	6.893	tap_A_OBUF[11]
				tap_A_OBUF[11]_inst/I
	OBUF (Prop_obuf_I_O)	2.634	9.528 r	tap_A_OBUF[11]_inst/O
	net (fo=0)	0.000	9.528	tap_A[11]
				tap_A[11] (OUT)
(clock axis_clk rise edge)				
	clock pessimism	12.000	12.000 r	
	clock uncertainty	0.000	12.000	
	output delay	-0.035	11.965	
		-2.400	9.565	
	required time		9.565	
	arrival time		-9.528	
	slack		0.037	

Fig15. Critical path

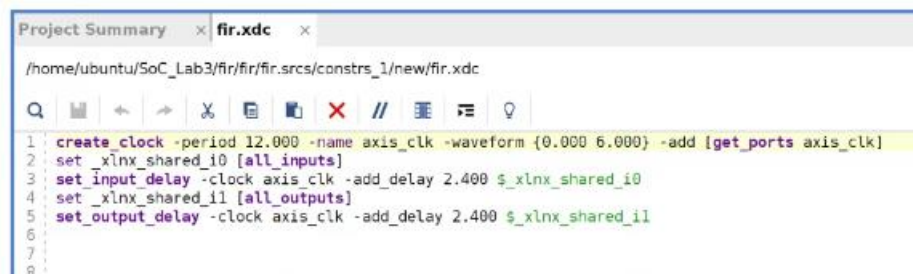

```
Project Summary x fir.xdc x
/home/ubuntu/SoC_Lab3/fir/fir.srsrcs/constrs_1/new/fir.xdc
1 create_clock -period 12.000 -name axis_clk -waveform {0.000 6.000} -add [get_ports axis_clk]
2 set_xlnx_shared_i0 [all_inputs]
3 set_input_delay -clock axis_clk -add_delay 2.400 $xlnx_shared_i0
4 set_xlnx_shared_i1 [all_outputs]
5 set_output_delay -clock axis_clk -add_delay 2.400 $xlnx_shared_i1
6
7
8
```

Fig16. Synthesize Constraint

[https://github.com/Chih-Ling-Wu/SoC\\_Lab3.git](https://github.com/Chih-Ling-Wu/SoC_Lab3.git)